




TRIP CIRCUITS AND SUPERVISION AND CORRECT CIRCUITRY

E-mail: rgh@rodhughesconsulting.com
Office: +61 8 7127 6357
Mobile: +61 419 845 253
Web: www.rodhughesconsulting.com
Skype: rodhughes-consult
LinkedIn: <https://www.linkedin.com/in/rodneyghughes>
Address: PO Box 757
Blackwood
SA 5051
Australia
A.B.N. 64 137 442 089



General Trip Circuit

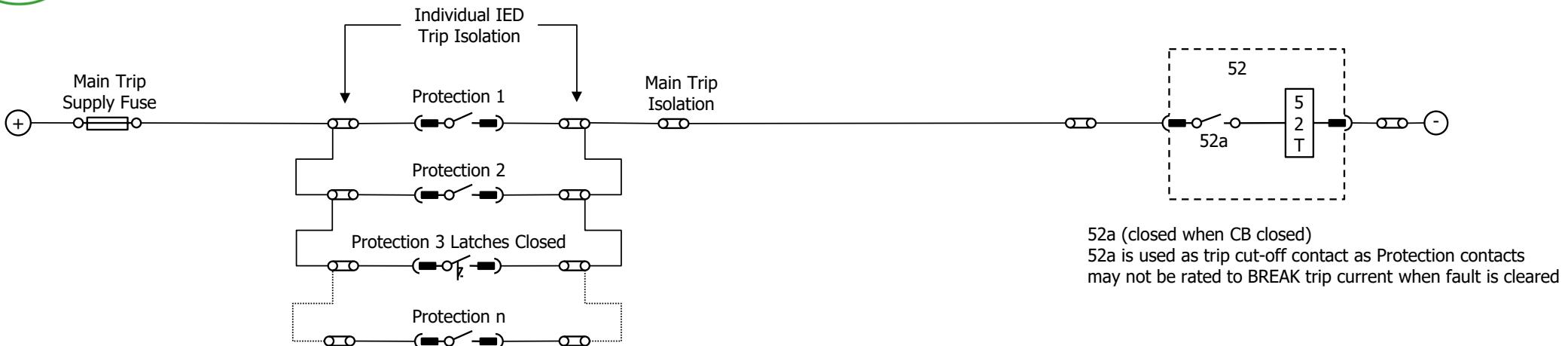


Protections contacts are generally self-resetting contacts.
When the fault condition is cleared by the CB opening, the protection function resets and its contact opens.

Protection 3 is shown with Latched Trip contact
Consider Protection 3 operates but CB fails to clear the fault as a CB Fail condition.
CB Fail should trip upstream breaker, but Protection 3 remains operated and 52a remains closed.
As such, 52T trip coil is permanently energized and may burn out!




Lockout Close Circuits

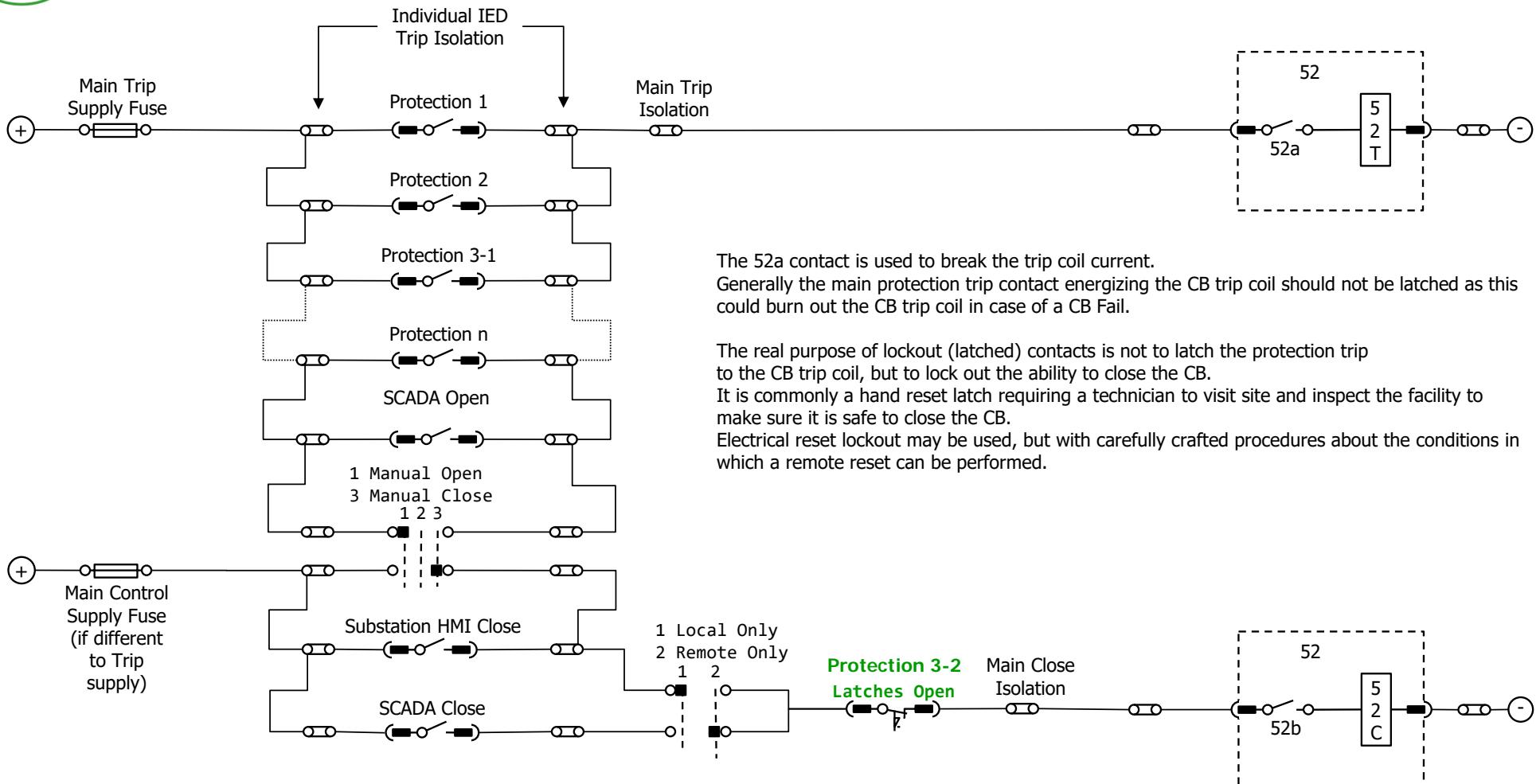




Trip Supervision

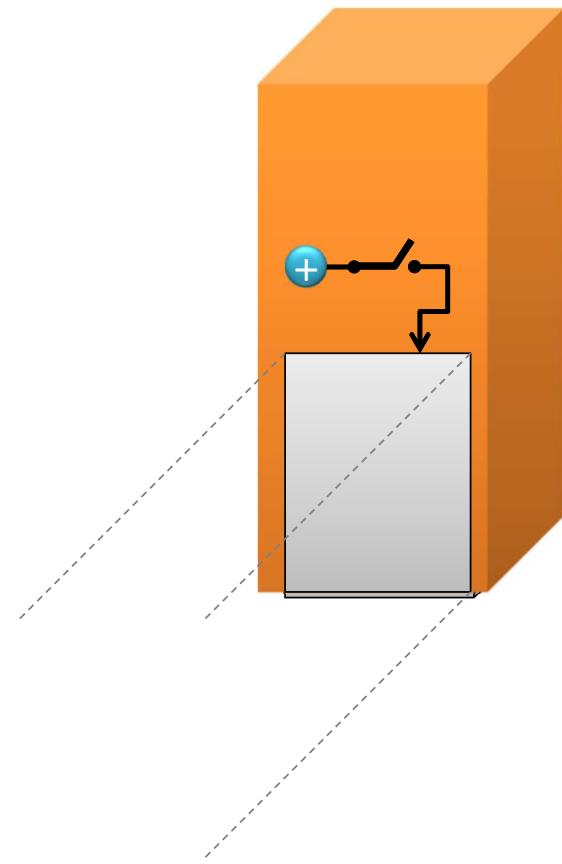- ↗ Supervision must not cause CB trip
- ↗ Must cater for CB open/closed change over time
- ↗ DC undervoltage monitor
- ↗ CB connection monitor
 - ★ Practical for withdrawable switchgear
 - ★ Verify plug has connected
 - ★ Does not verify 52T “pin” in connector is made






Connection Monitor

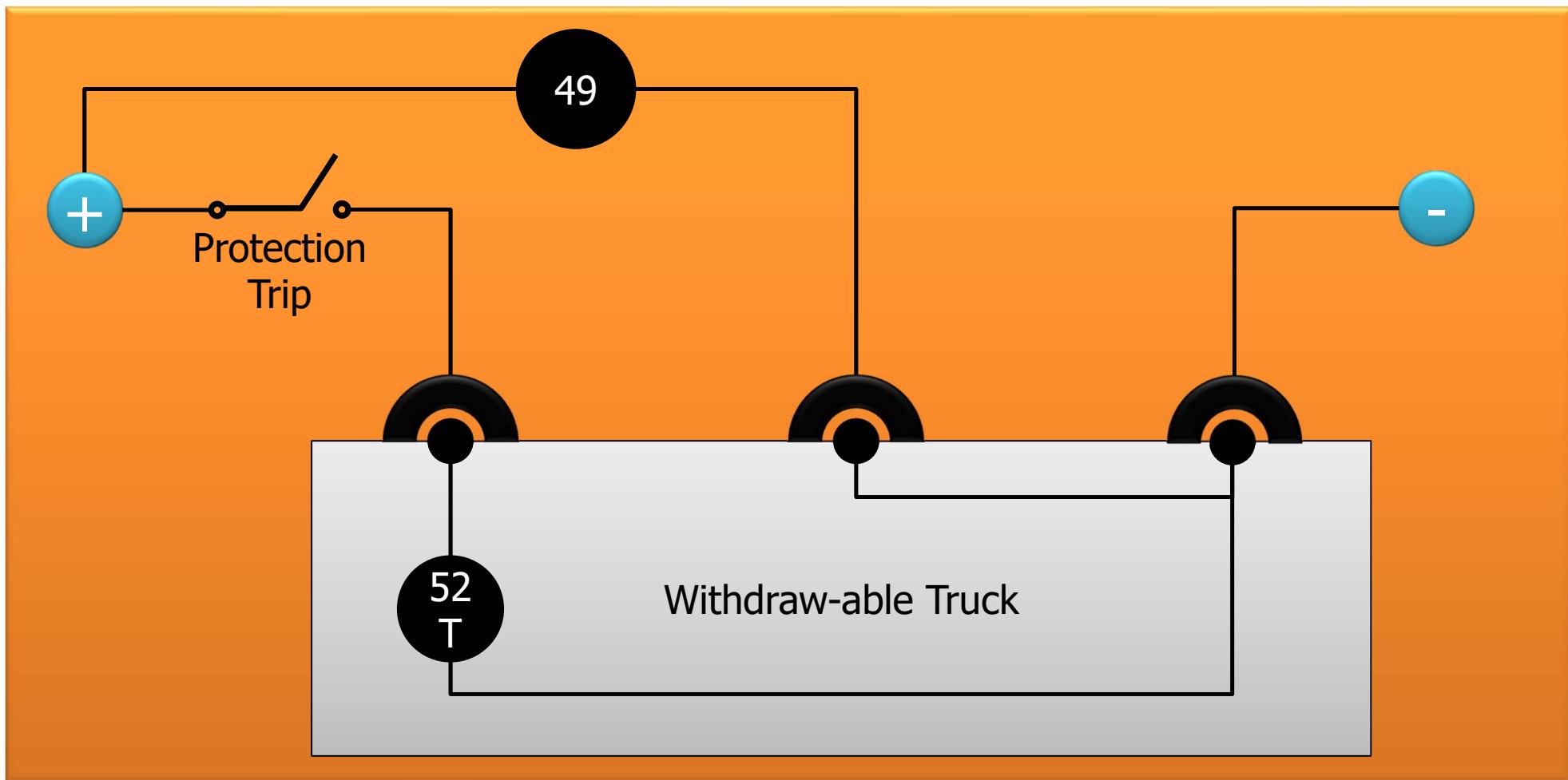



Trip Supply Monitor

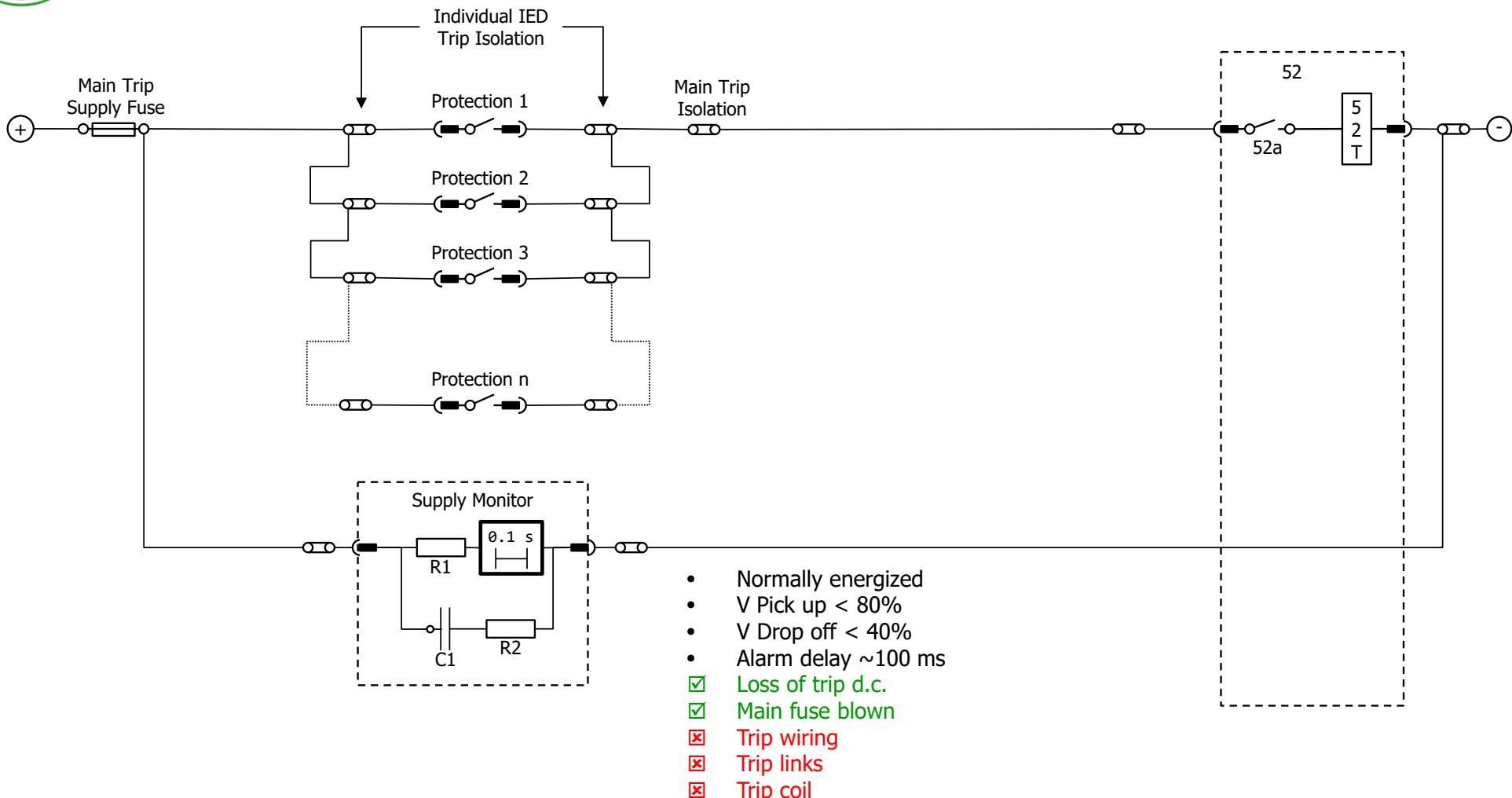




COIL-BASED TRIP CIRCUIT SUPERVISION




General Trip Circuit: 'X' Protection

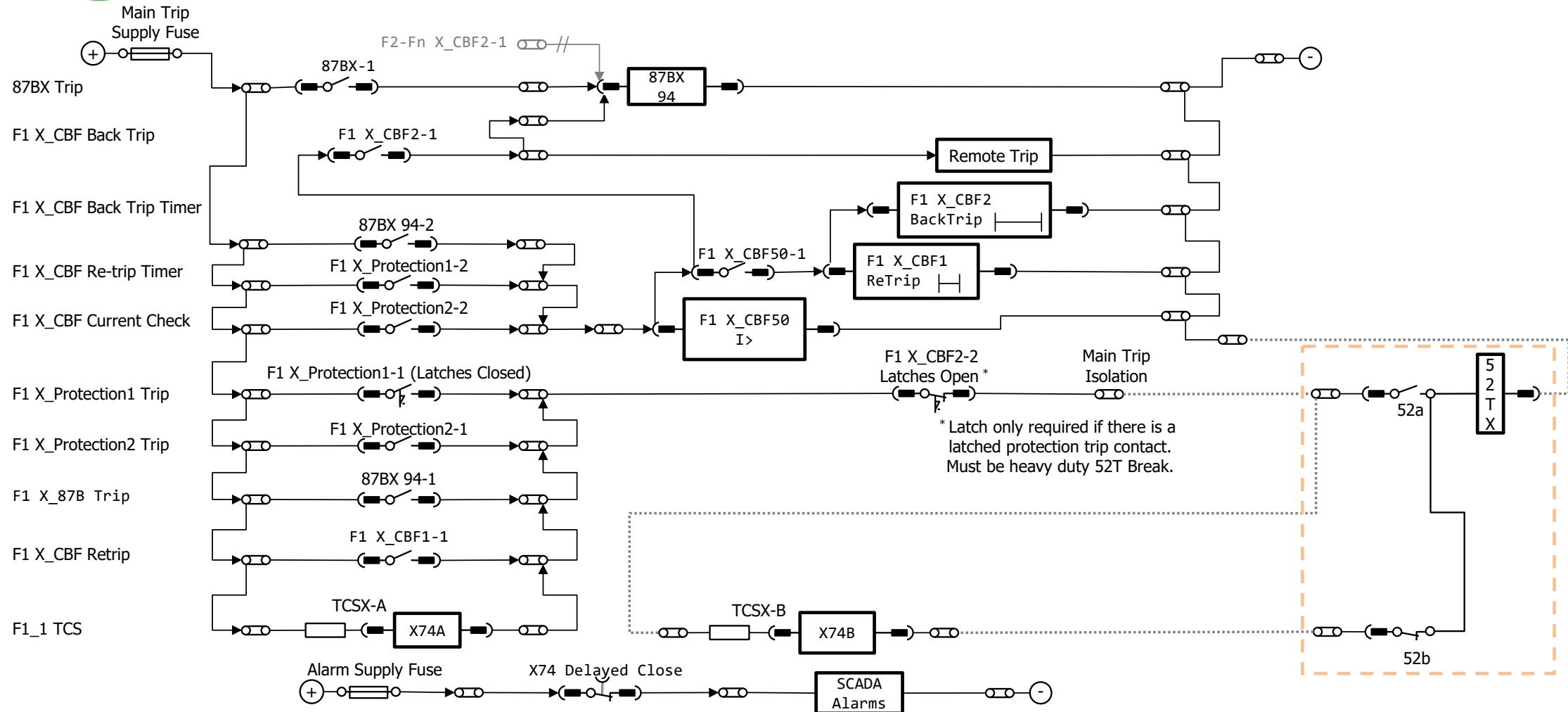




Supervised Wiring: CB Closed

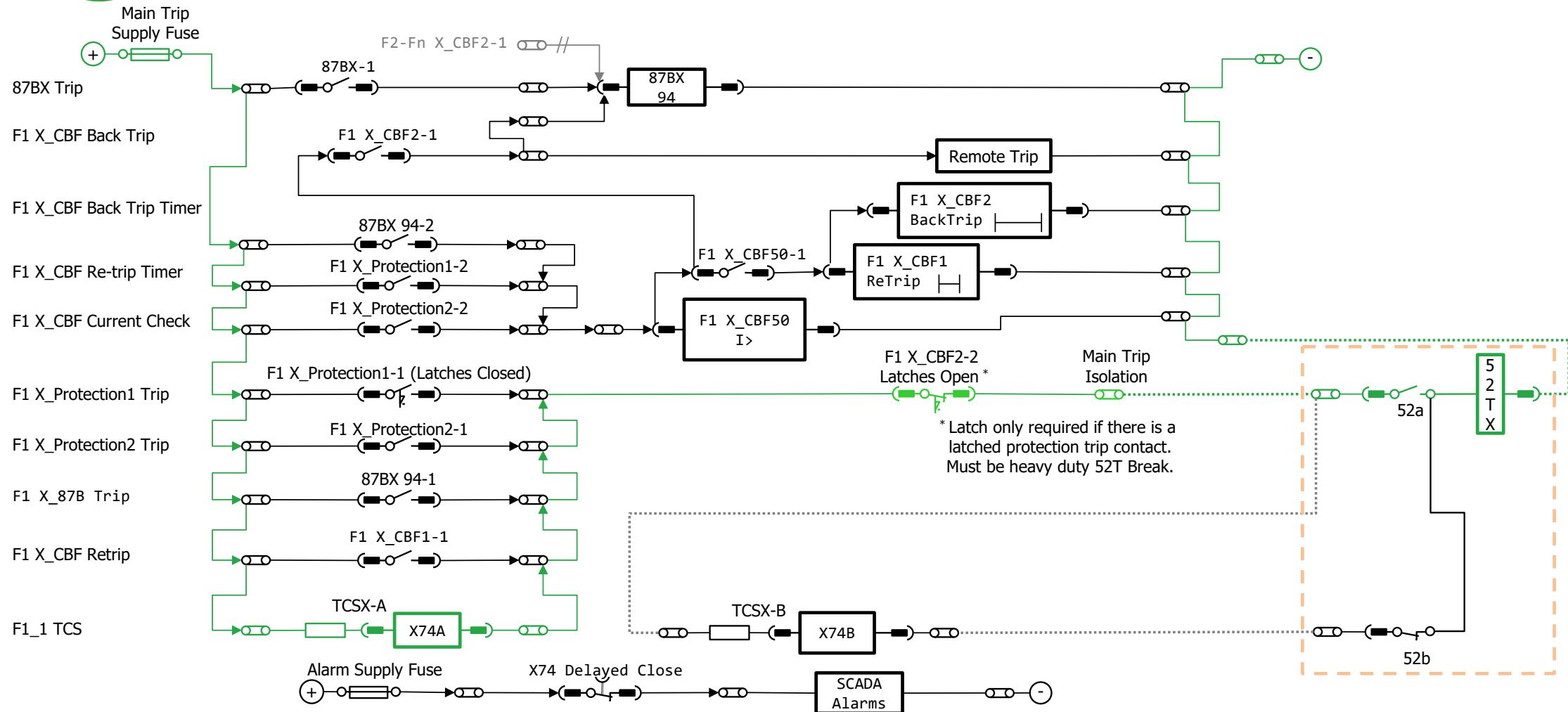

Supervised Wiring: Pre-Close, CB Open

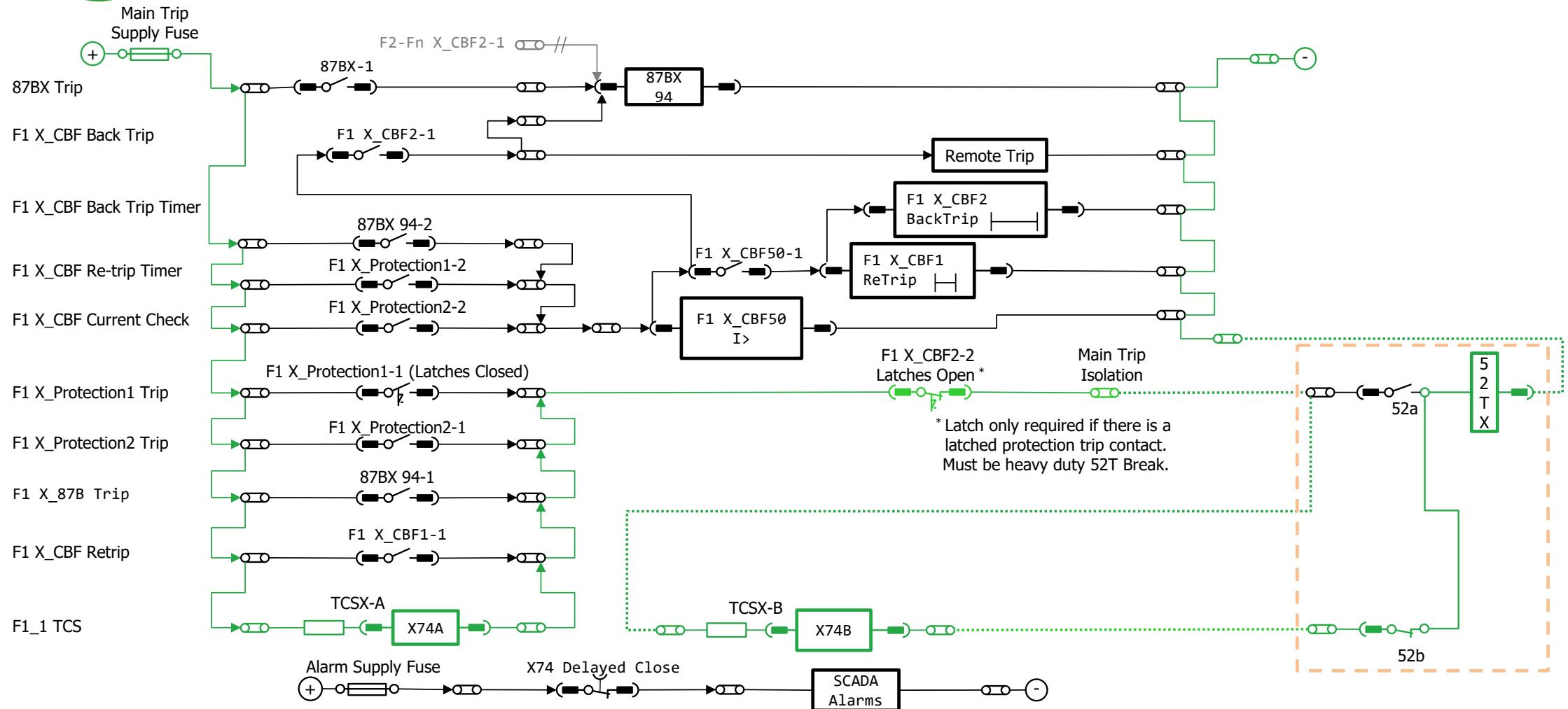




- TCS cannot “supervise” correct mechanical operation of 52a or 52b
 - ✚ Only confirms if the contact is in the correct position relative to the CB at that instant
 - ✚ Cannot predict contact will change state when CB changes state
- TCS is no basis of NOT doing regular CB maintenance




Incorrect TCS Location (1)

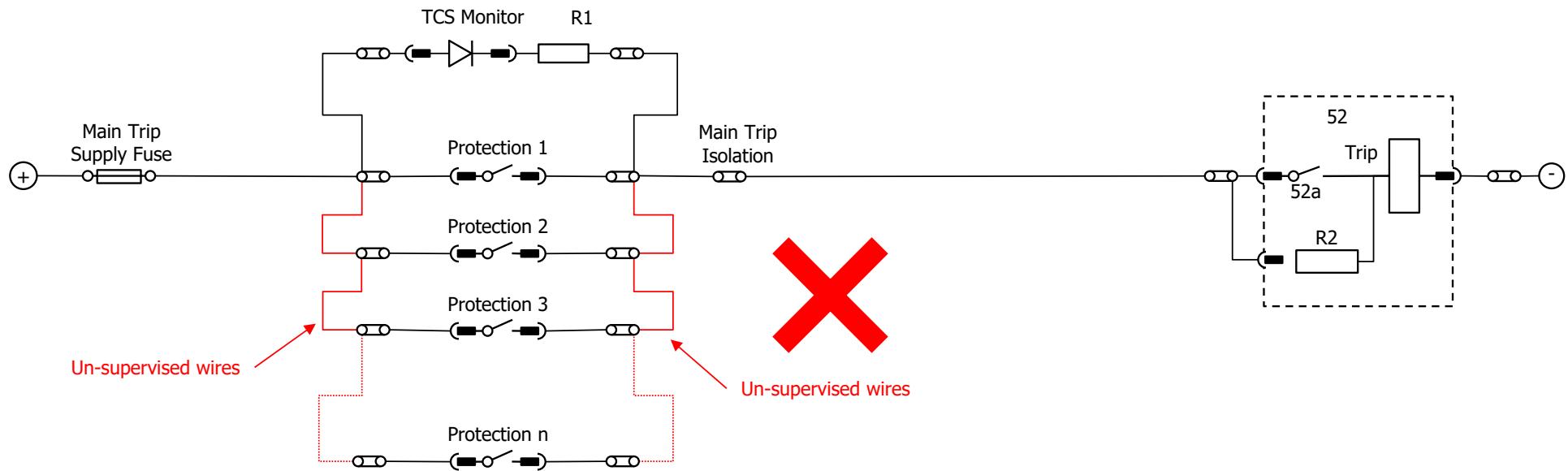




Incorrect TCS Location (2)

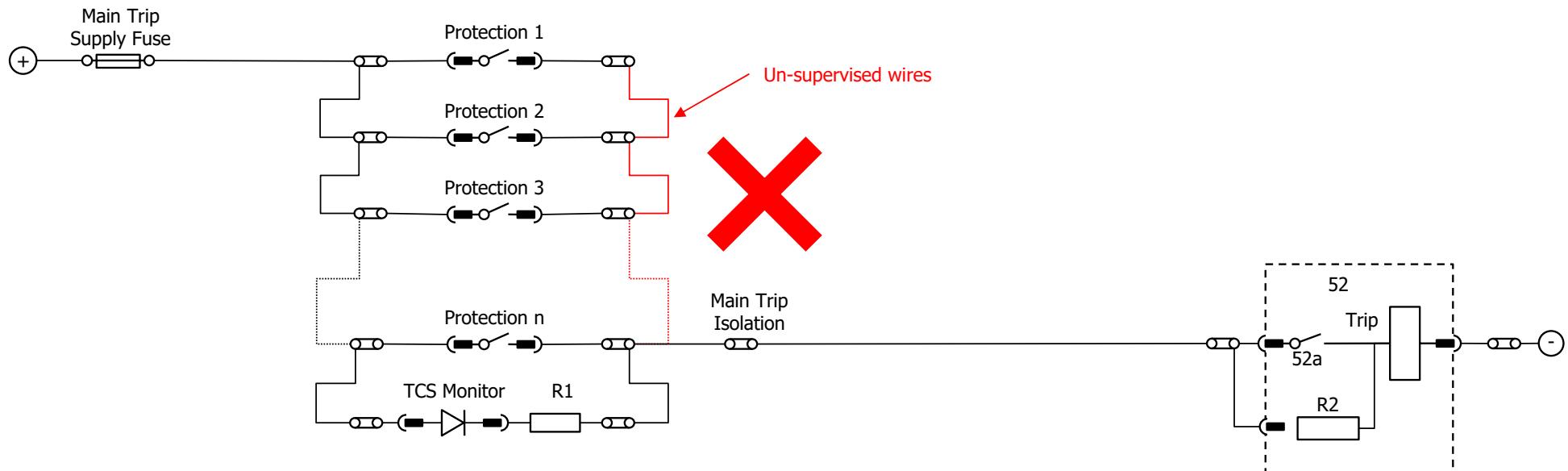



Correct TCS Location

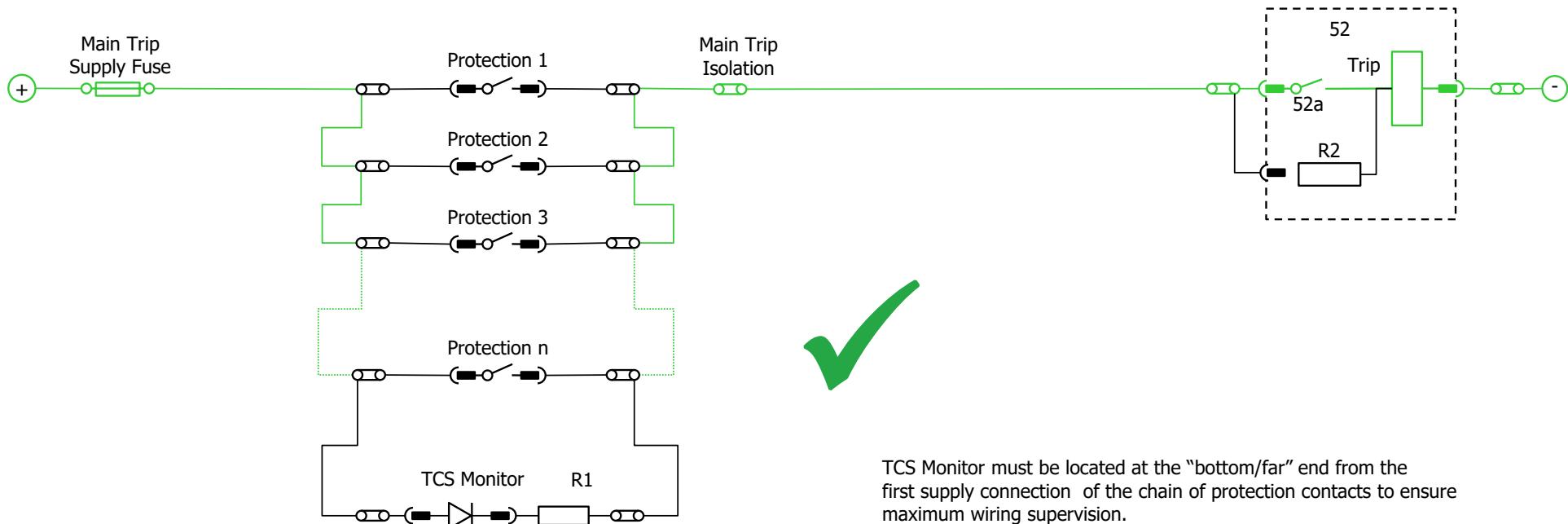


TCS Monitor must be located at the "bottom/far" end from the first supply connection of the chain of protection contacts to ensure maximum wiring supervision.



DIFFERENT SCHEMES




TCS for CB Closed

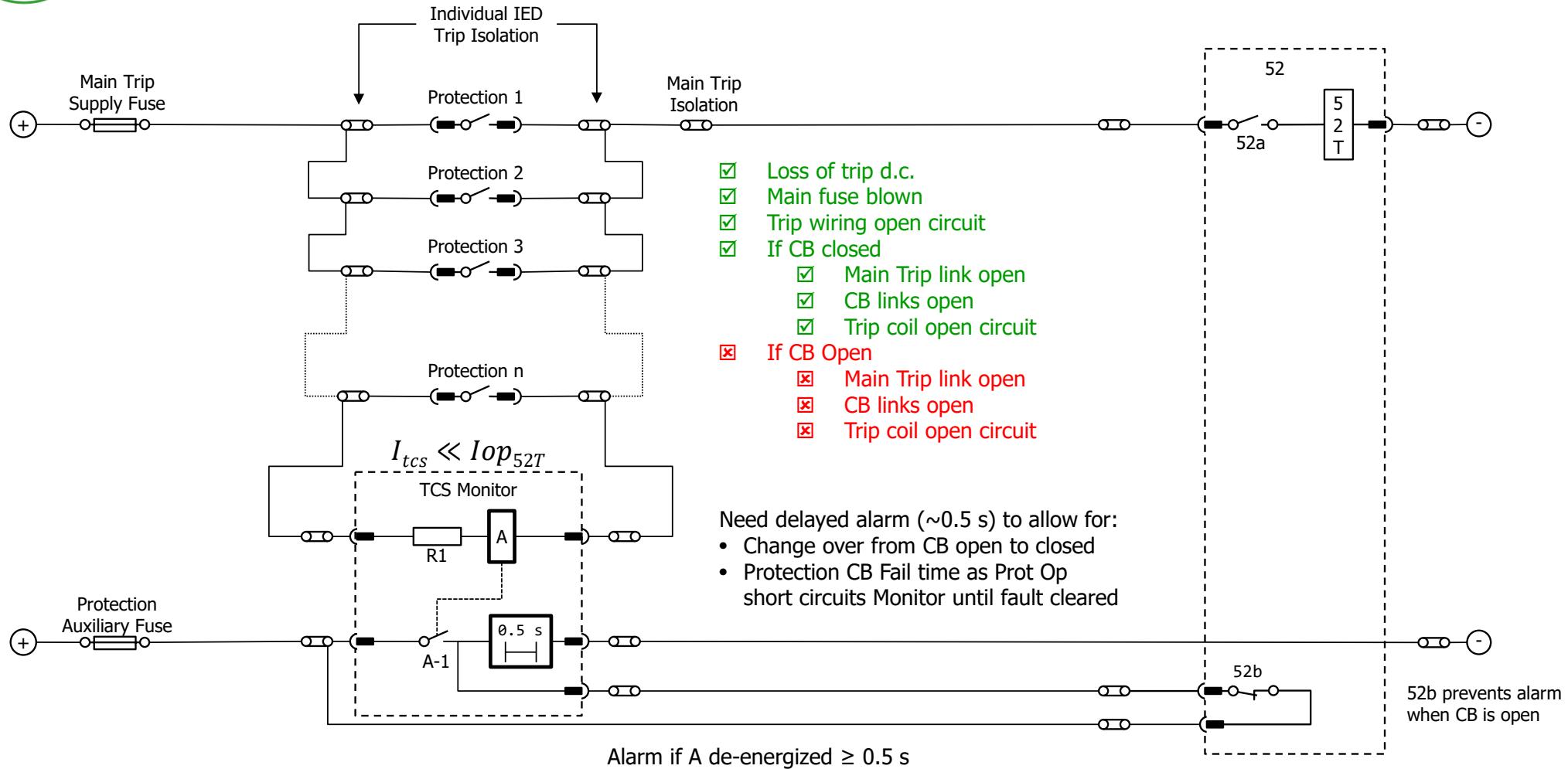




Full Relay-Monitor TCS

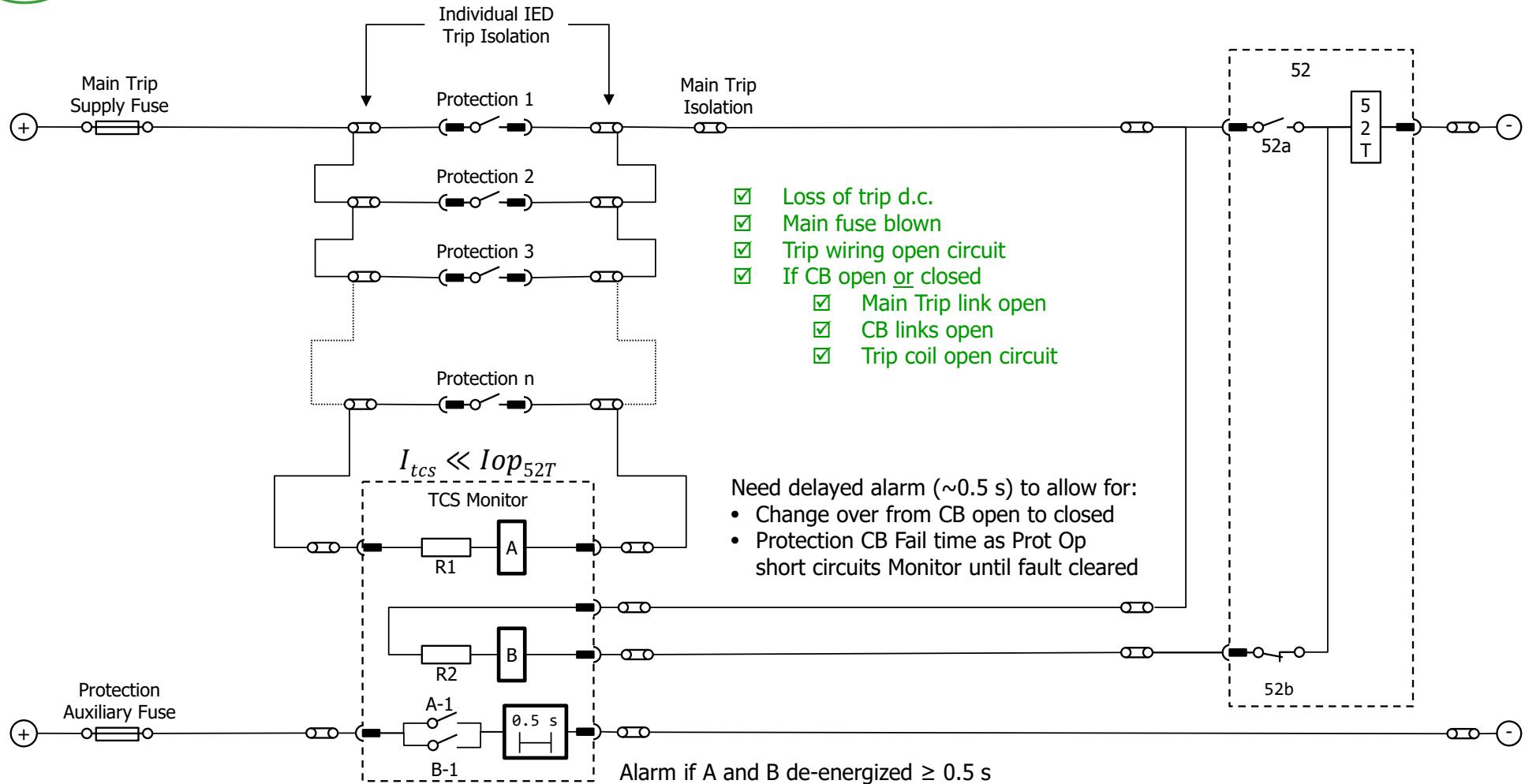




Full TCS: CB Closed

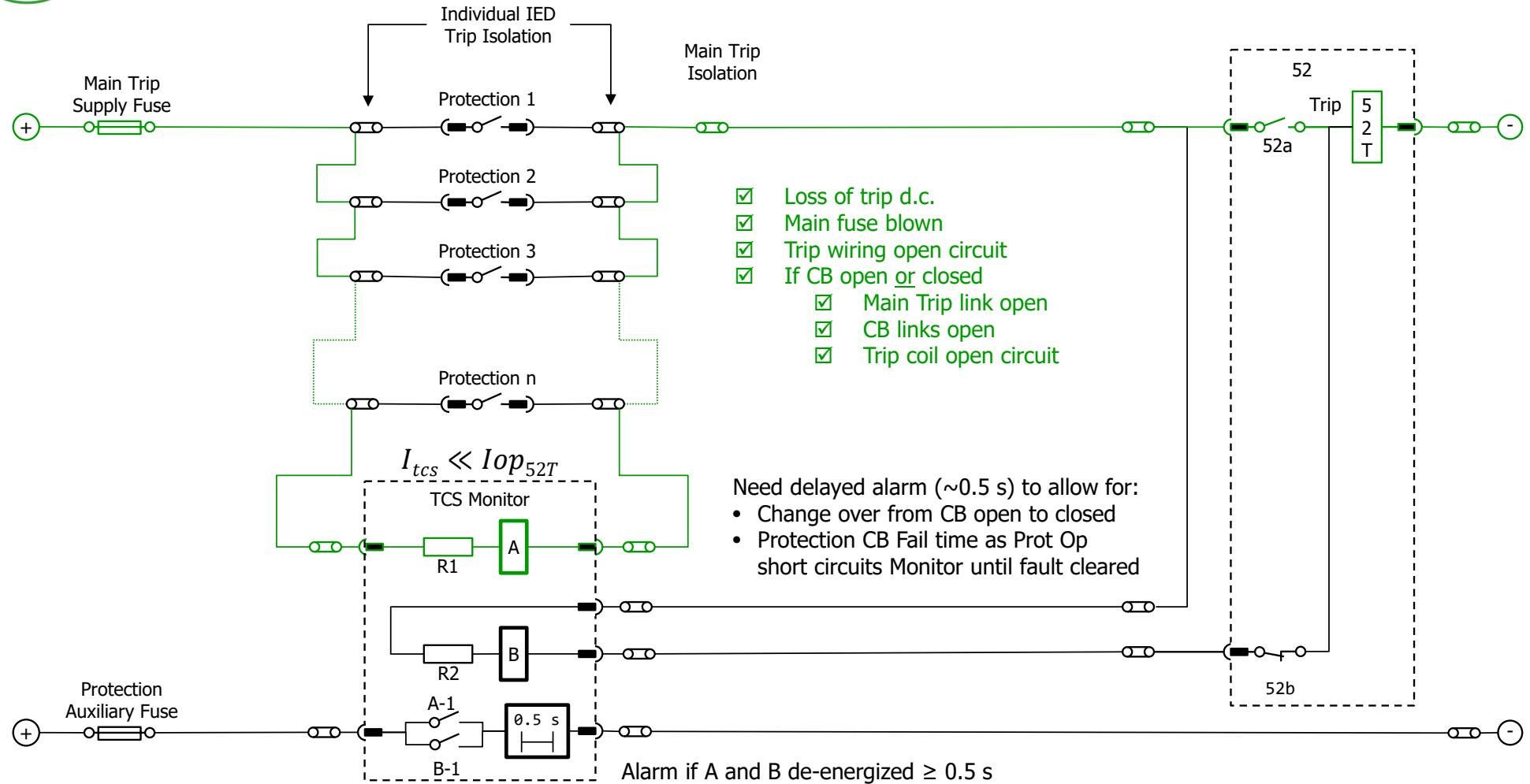




Full TCS: CB closed, Prot operated

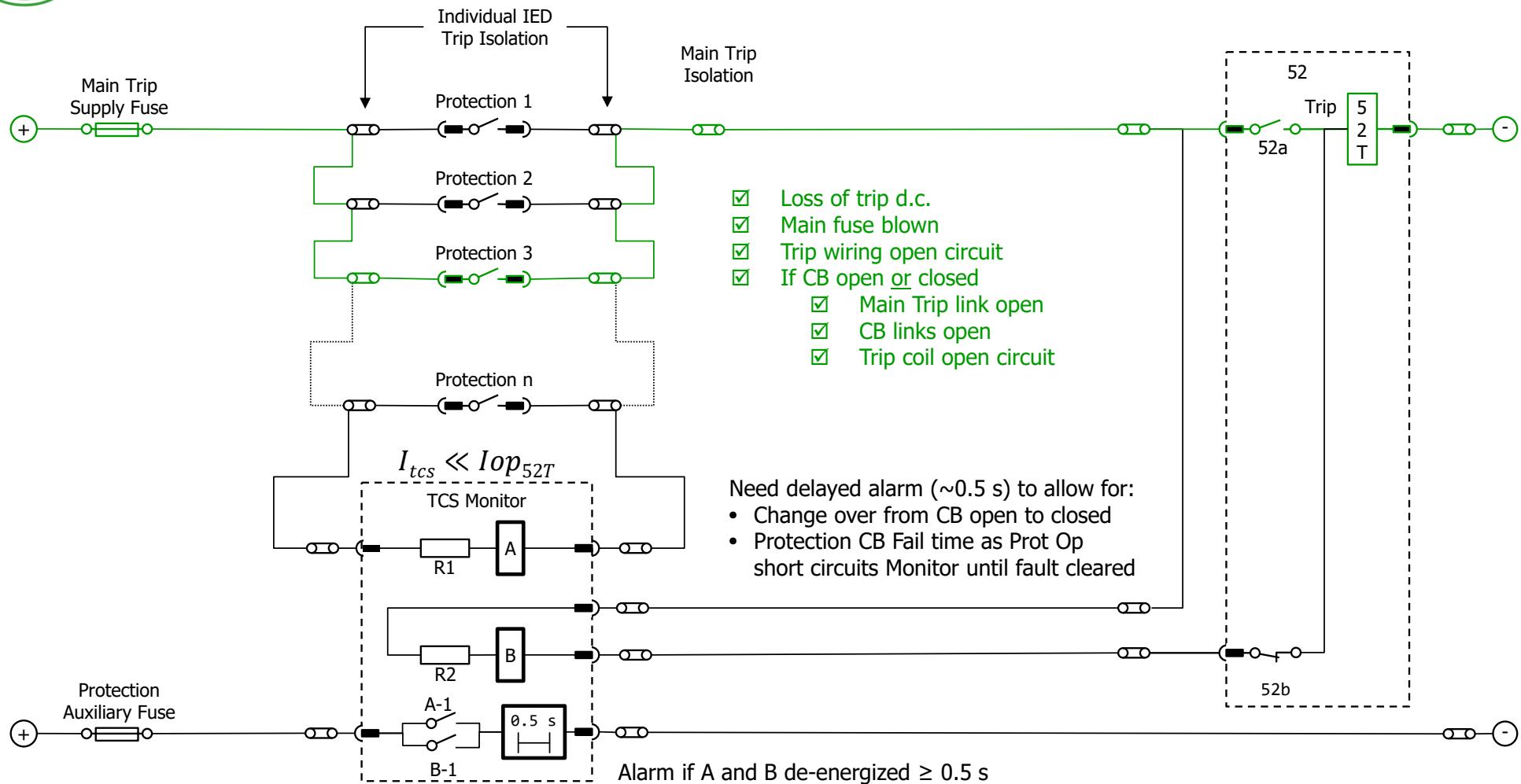




Full TCS: CB Open

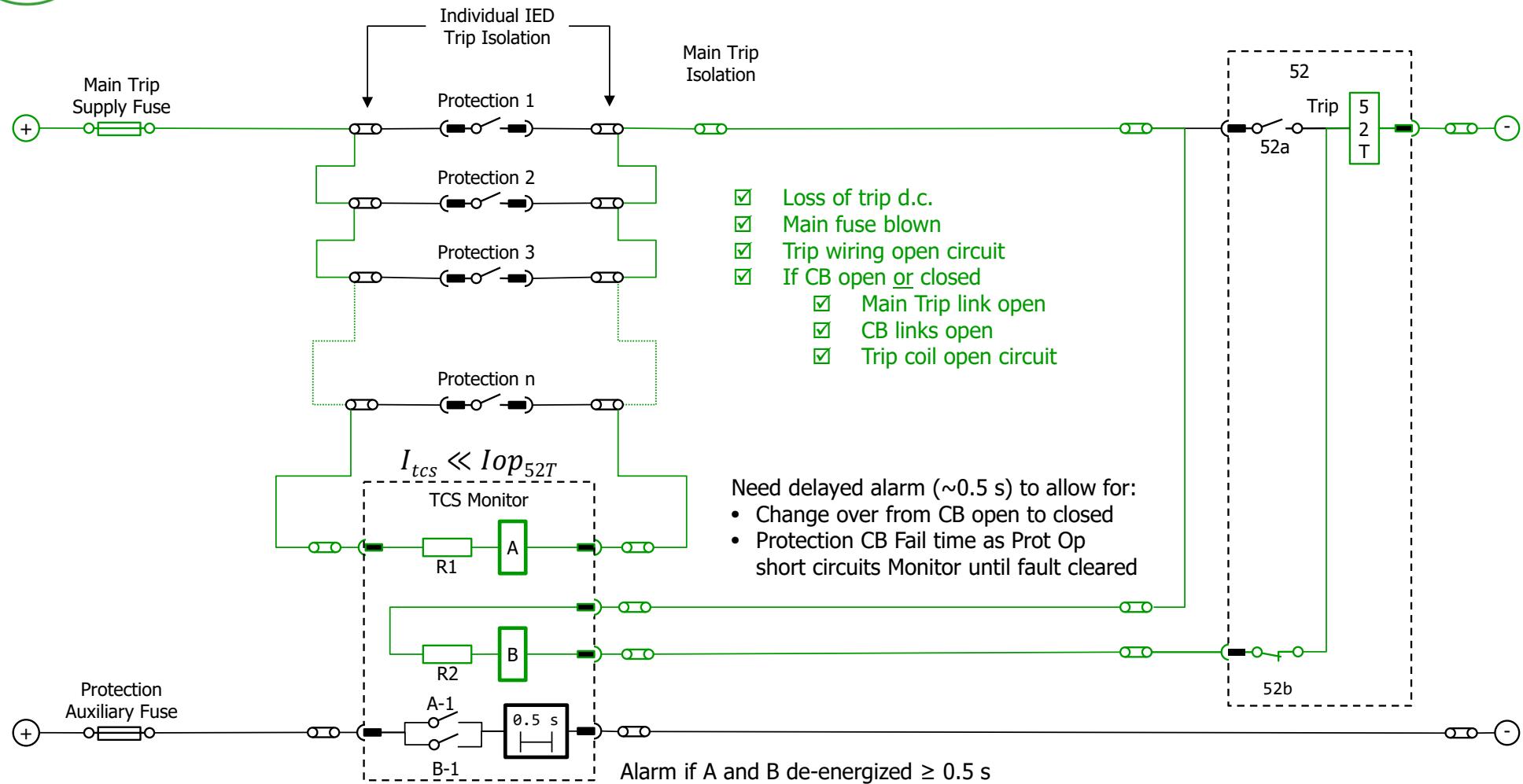




Full Opto-Monitor TCS: Two Opto

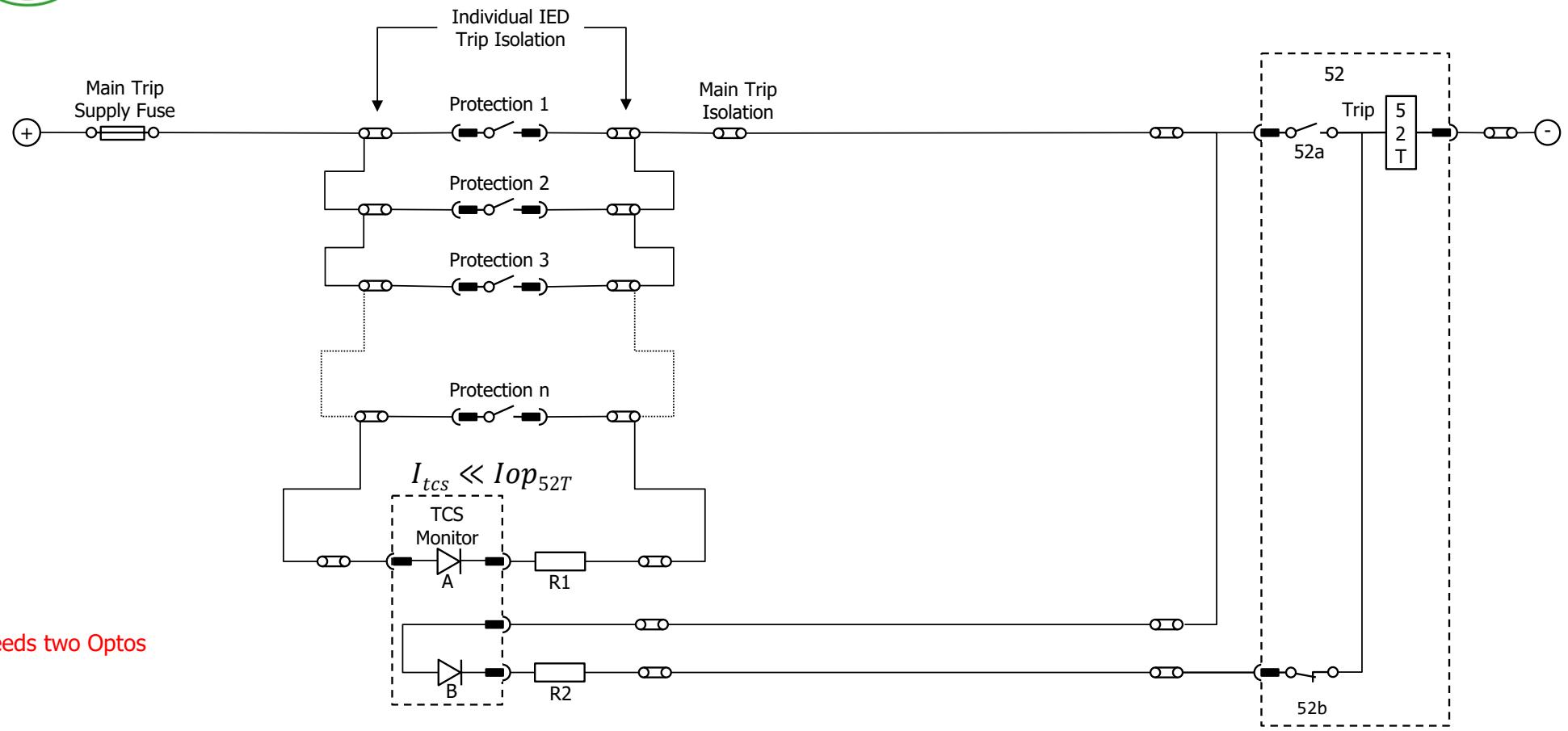

Alarm if A and B de-energized ≥ 0.5 s




Full Opto-Monitor TCS: One Opto

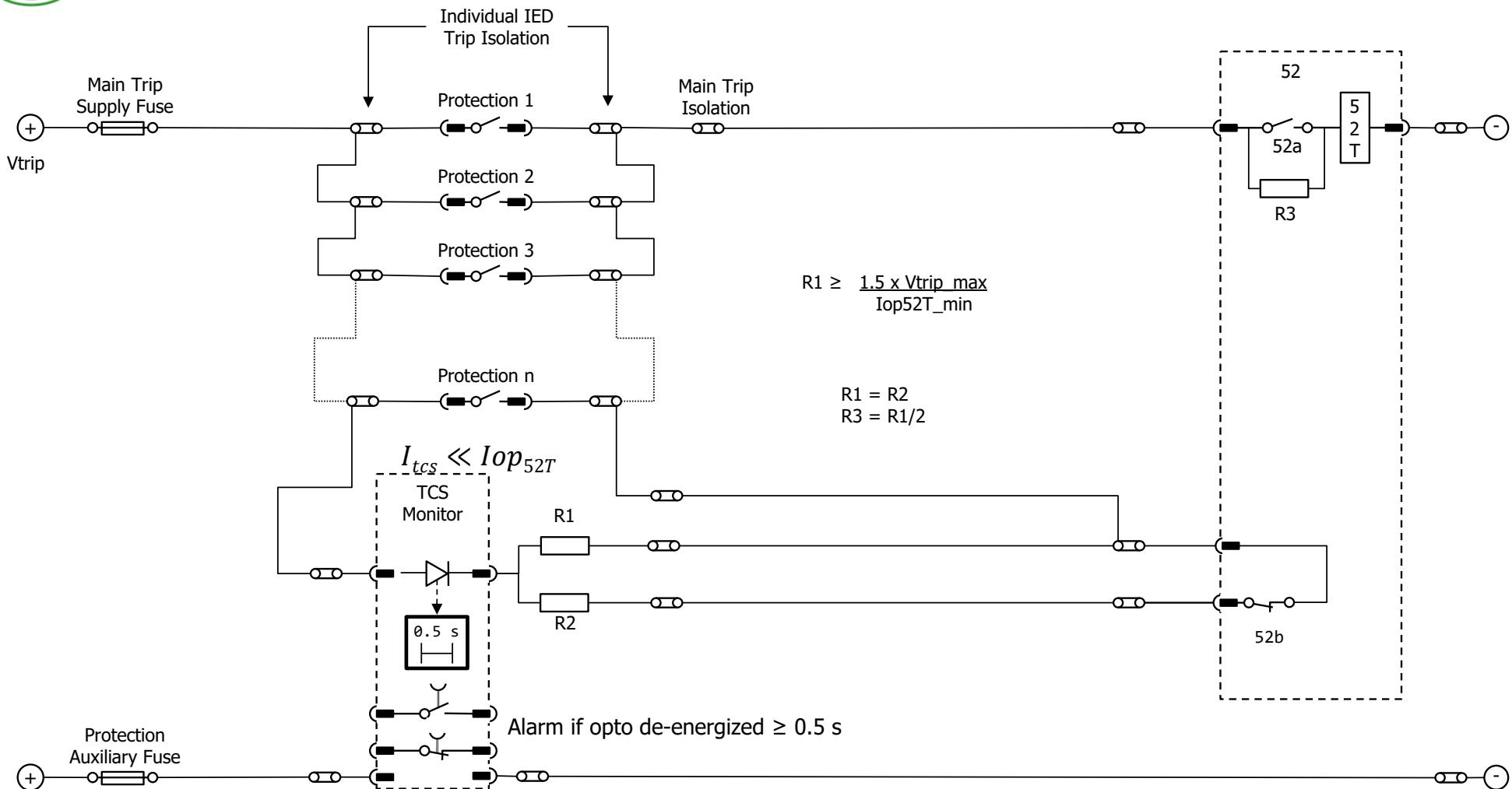




One TCS Opto: CB Closed

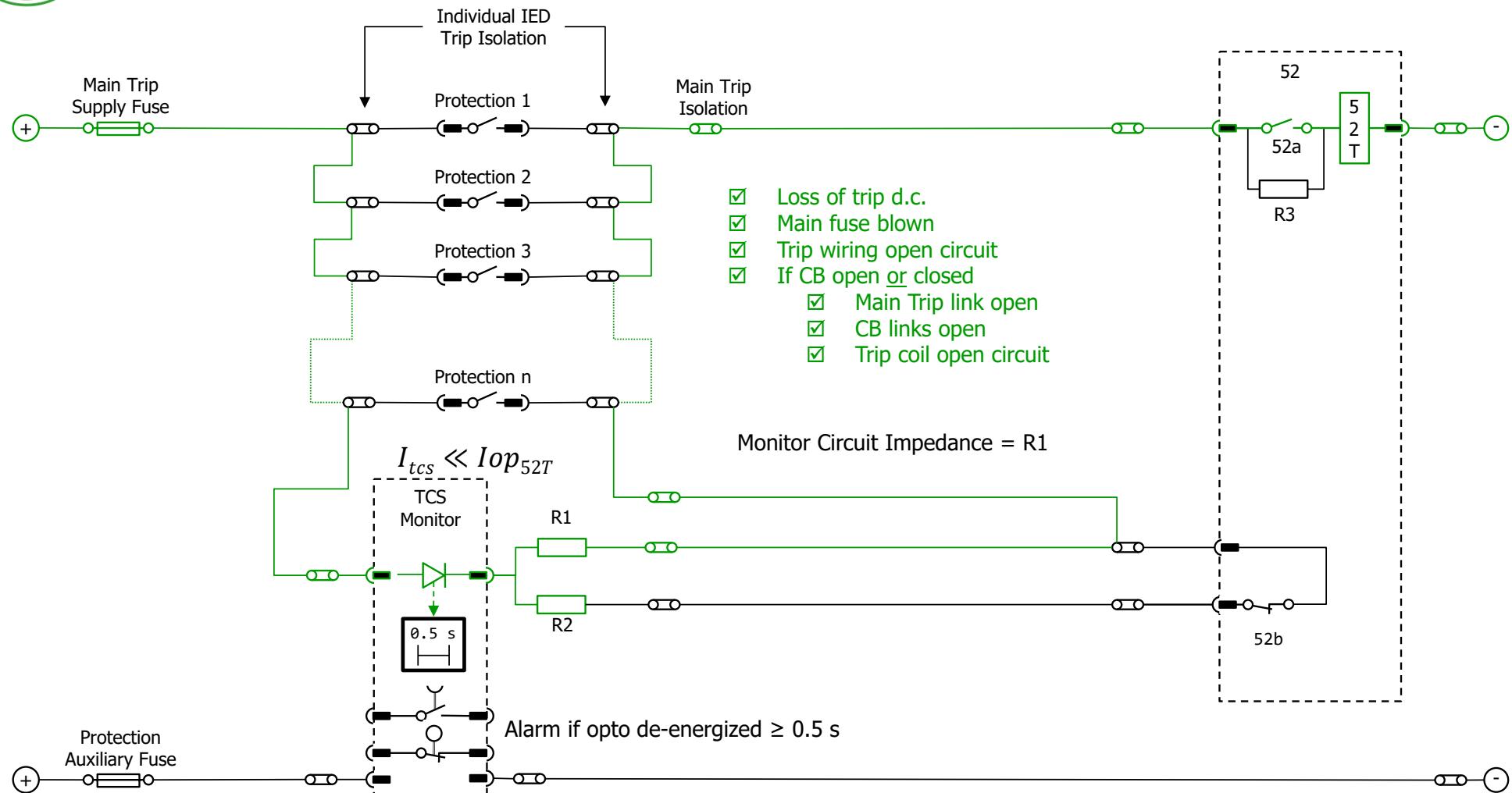




One TCS Opto: CB Open

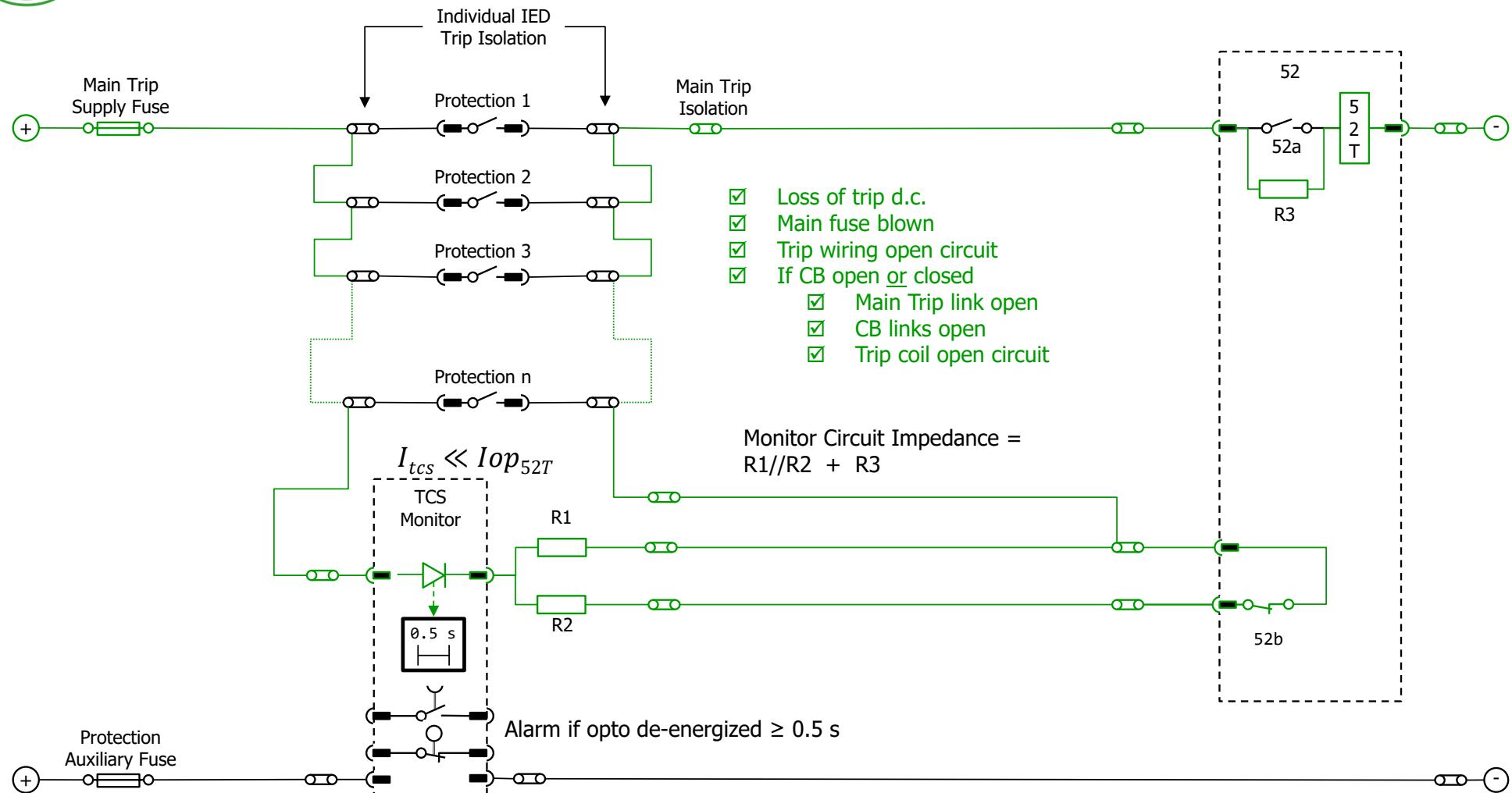



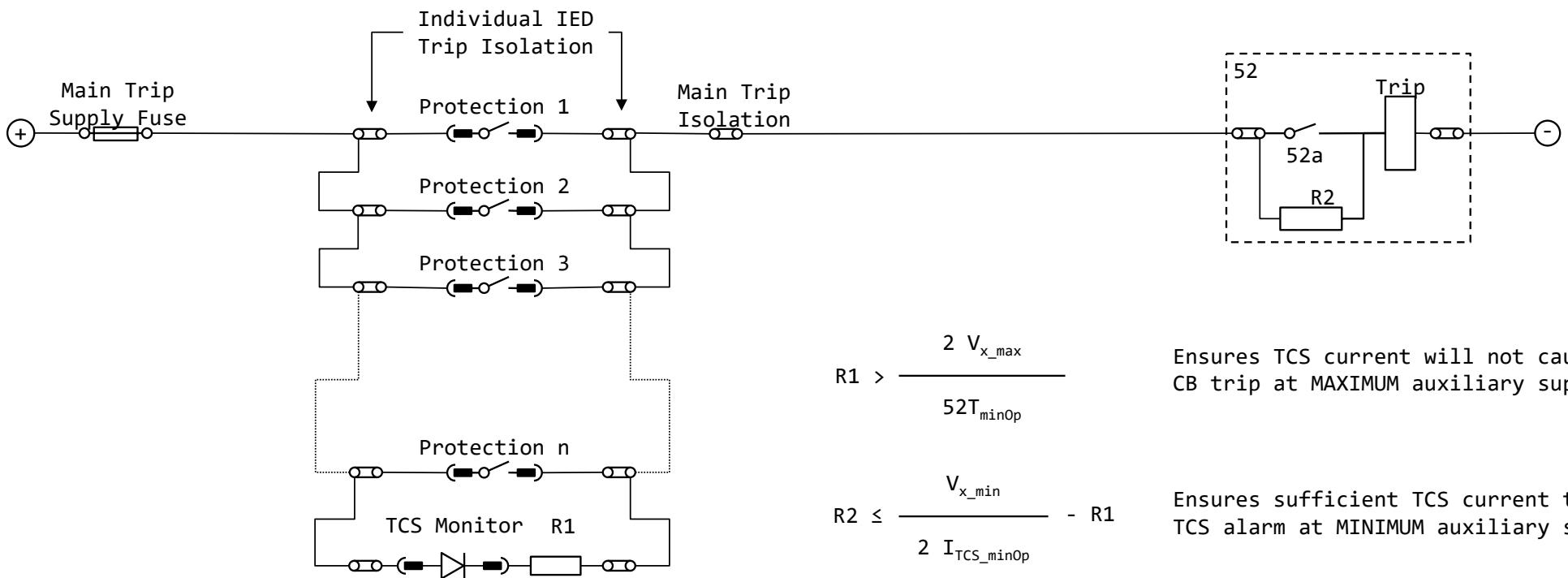Single Opto, Single Wire Single CB Aux Contact Full TCS



$$R1 > \frac{2 V_{x_max}}{52T_{minOp}}$$

Ensures TCS current will not cause CB trip at MAXIMUM auxiliary supply

$$R2 \leq \frac{V_{x_min}}{2 I_{TCS_minOp}} - R1$$

Ensures sufficient TCS current to prevent TCS alarm at MINIMUM auxiliary supply


Note: TCS is normally energised

When protection operates, TCS is short circuited and will therefore de-energise

But ... Is this really what you want?




CB Fail Triggered

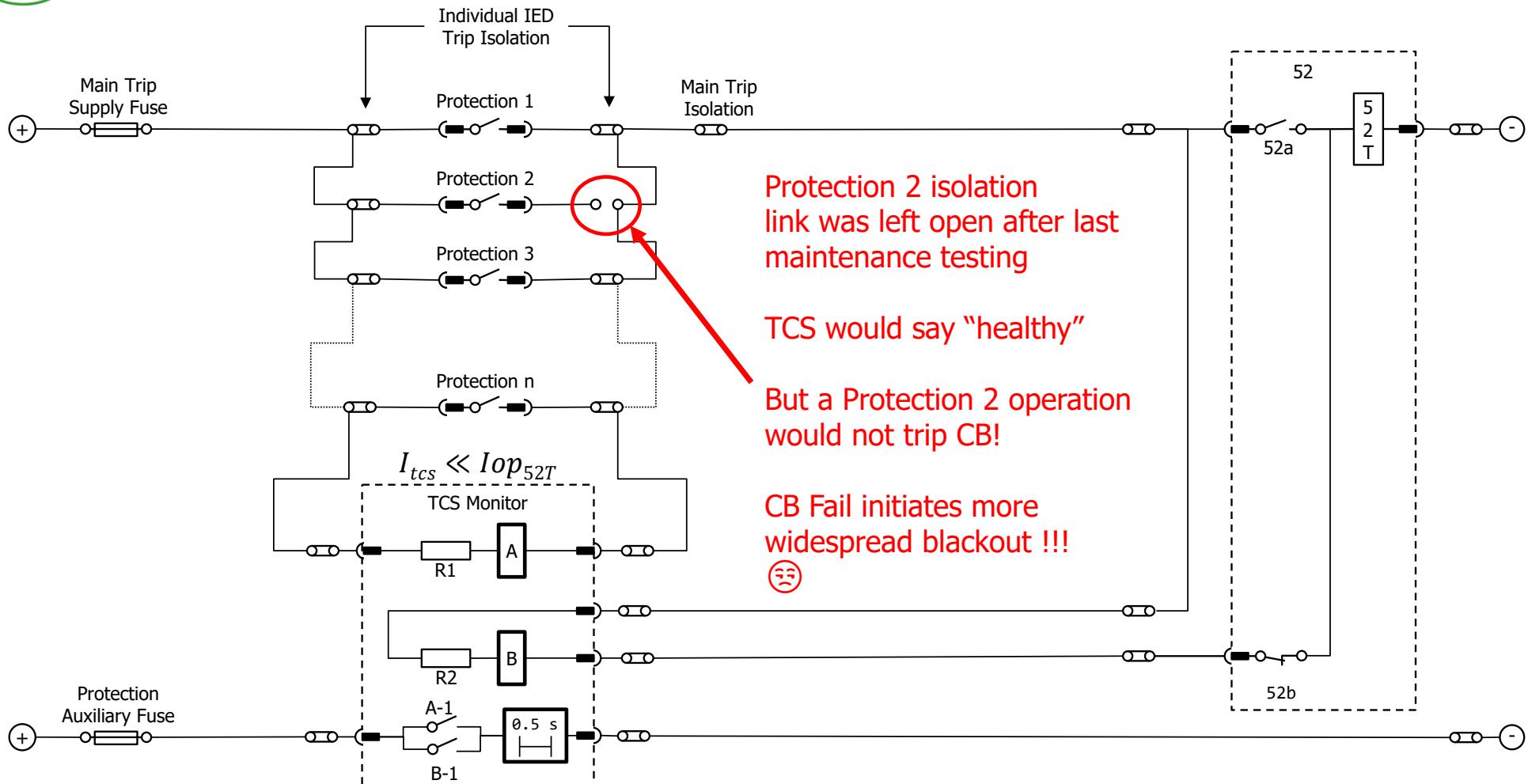



CB Fail Local Re-trip

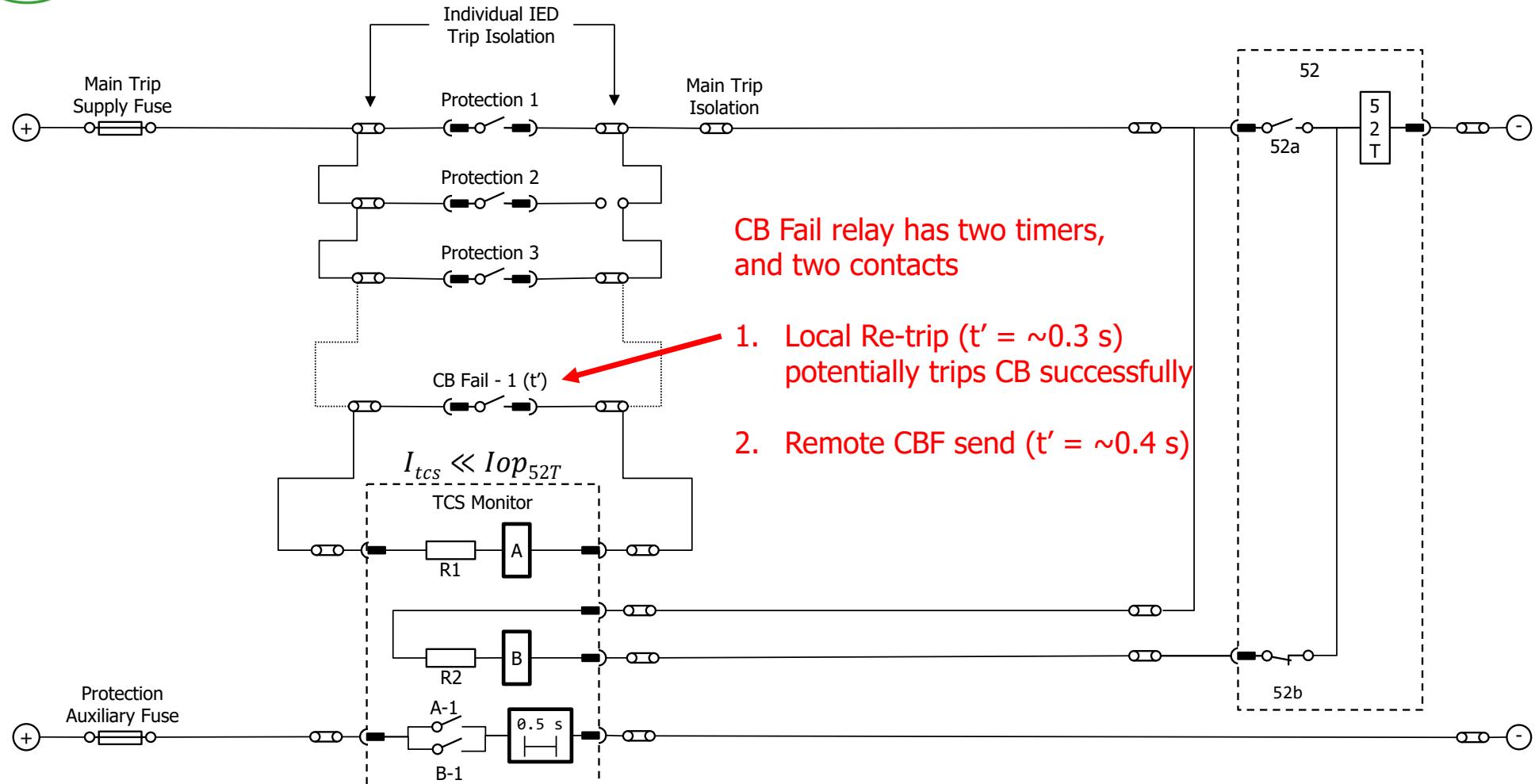



E-mail: rgh@rodhughesconsulting.com
Office: +61 8 7127 6357
Mobile: +61 419 845 253
Web: www.rodhughesconsulting.com
Skype: rodhughes-consult
LinkedIn: <https://www.linkedin.com/in/rodneyghughes>
Address: PO Box 757
Blackwood
SA 5051
Australia
A.B.N. 64 137 442 089